

# Revision Pack Topic P2- Electricity

	R/A/G
<b>Current, potential difference and resistance</b>	
<b>Standard circuit diagram symbols</b>	
<p>  switch (open)       lamp   switch (closed)       fuse   cell       voltmeter   battery       ammeter   diode       thermistor   resistor       LDR   variable resistor   LED         </p>	
<b>Electrical charge and current</b>	
For electrical charge to flow through a closed circuit the circuit must include a source of potential difference.	
<p>Electric current is a flow of electrical charge.</p> <p>The size of the electric current is the rate of flow of electrical charge.</p> <p>Charge flow, current and time are linked by the equation: charge flow = current × time</p> <p><b>Q = I t</b></p> <p>charge flow, Q, in coulombs, C current, I, in amperes, A, time, t, in seconds, s</p> <p>A current has the same value at any point in a single closed loop.</p>	
<b>Current, resistance and potential difference</b>	
The current (I) through a component depends on both the resistance (R) of the component and the potential difference (V) across the component. The greater the resistance of the component the smaller the current for a given potential difference (pd) across the component.	
<p>Current, potential difference or resistance can be calculated using the equation:</p> <p>potential difference = current × resistance</p> <p><math>V = I R</math> potential difference, V, in volts, V current, I, in amperes, A, resistance, R, in ohms, <math>\Omega</math></p>	
<p>Use circuit diagrams to set up and check appropriate circuits to investigate the factors affecting the resistance of electrical circuits.</p> <p>This should include:</p> <ul style="list-style-type: none"> <li>• the length of a wire at constant temperature</li> <li>• combinations of resistors in series and parallel.</li> </ul>	
<b>Resistors</b>	

# Revision Pack Topic P2- Electricity

<p>For some resistors, the value of R remains constant but that in others it can change as the current changes. The current through an ohmic conductor (at a constant temperature) is directly proportional to the potential difference across the resistor. This means that the resistance remains constant as the current changes.</p> <p>The resistance of components such as lamps, diodes, thermistors and LDRs is not constant; it changes with the current through the component. The resistance of a filament lamp increases as the temperature of the filament increases.</p> <p>The current through a diode flows in one direction only.</p> <p>The diode has a very high resistance in the reverse direction.</p>	
<p>The resistance of a thermistor decreases as the temperature increases.</p> <p>The resistance of an LDR decreases as light intensity increases.</p>	
<p><b>Required practical activity 16:</b> use circuit diagrams to construct appropriate circuits to investigate the I-V characteristics of a variety of circuit elements, including a filament lamp, a diode and a resistor at constant temperature.</p>	
<p><b>Series and parallel circuits</b></p>	
<p>There are two ways of joining electrical components, in series and in parallel. Some circuits include both series and parallel parts.</p> <p>For components connected in series:</p> <ul style="list-style-type: none"> <li>• there is the same current through each component</li> <li>• the total potential difference of the power supply is shared between the components</li> <li>• the total resistance of two components is the sum of the resistance of each component.</li> </ul>	
<p><math>R_{\text{total}} = R_1 + R_2</math> resistance, R, in ohms, <math>\Omega</math></p> <p>For components connected in parallel:</p> <ul style="list-style-type: none"> <li>• the potential difference across each component is the same</li> <li>• the total current through the whole circuit is the sum of the currents through the separate components</li> <li>• the total resistance of two resistors is less than the resistance of the smallest individual resistor.</li> </ul>	
<p><b>Domestic uses and safety</b></p>	
<p><b>Direct and alternating potential difference</b></p>	
<p>Mains electricity is an ac supply. In the United Kingdom the domestic electricity supply has a frequency of 50 Hz and is about 230 V.</p>	
<p>Most electrical appliances are connected to the mains using three core cable. The insulation covering each wire is colour coded for easy identification:</p> <p>live wire - brown  neutral wire - blue  earth wire - green and yellow stripes. T</p> <p>he live wire carries the alternating potential difference from the supply. The neutral wire completes the circuit. The earth wire is a safety wire to stop the appliance becoming live. The potential difference between the live wire and earth (0 V) is about</p>	

# Revision Pack Topic P2- Electricity

230 V. The neutral wire is at, or close to, earth potential (0 V). The earth wire is at 0 V, it only carries a current if there is a fault.	
<b>Energy transfers</b>	
<b>Power</b>	
Students should be able to explain how the power transfer in any circuit device is related to the potential difference across it and the current through it, and to the energy changes over time: power = potential difference $\times$ current $P = V I$ power = current $^2 \times$ resistance $P = I^2 R$ power, P, in watts, W potential difference, V, in volts, V current, I, in amperes, A, resistance, R, in ohms, $\Omega$	
<b>Energy transfers in everyday appliances</b>	
Everyday electrical appliances are designed to bring about energy transfers. The amount of energy an appliance transfers depends on how long the appliance is switched on for and the power of the appliance. Work is done when charge flows in a circuit. The amount of energy transferred by electrical work can be calculated using the equation: energy transferred = power $\times$ time $E = P t$ energy transferred = charge flow $\times$ potential difference $E = Q V$ energy transferred, E, in joules, J power, P, in watts, W time, t, in seconds, s charge flow, Q, in coulombs, C potential difference, V, in volts, V	
<b>The National Grid</b>	
The National Grid is a system of cables and transformers linking power stations to consumers.	
Electrical power is transferred from power stations to consumers using the National Grid. Step-up transformers are used to increase the potential difference from the power station to the transmission cables then step-down transformers are used to decrease, to a much lower value, the potential difference for domestic use.	

## **Current and circuit symbols**

Define the term current and give the unit.

---

Define the term voltage and give the unit.

---

Define the term resistance and give the unit.

---

# Revision Pack Topic P2- Electricity

Give the equation used to calculate charge:


---

Match the terms below:

Current	Placed in parallel; measures the potential difference across a component
Potential difference	Flow of electric charge
Resistance	Component; resistance decreases as temperature increases
Voltmeter	Charge/ current moves in one direction around the circuit
Ammeter	Voltage; energy transferred per unit of charge
Direct current	Charge/ current changes direction
Alternating current	Placed in series; measures the current
Thermistor	Component; resistance decreases as intensity of light increases
LDR	Calculated using the equation $V \div I$
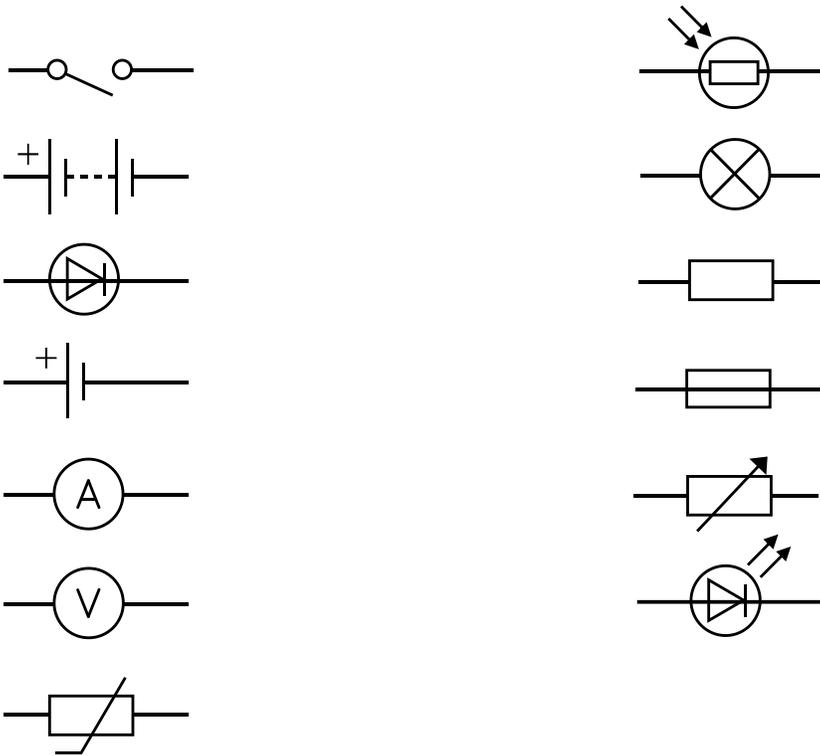
# Revision Pack Topic P2- Electricity


Label the circuit symbols with the correct word:


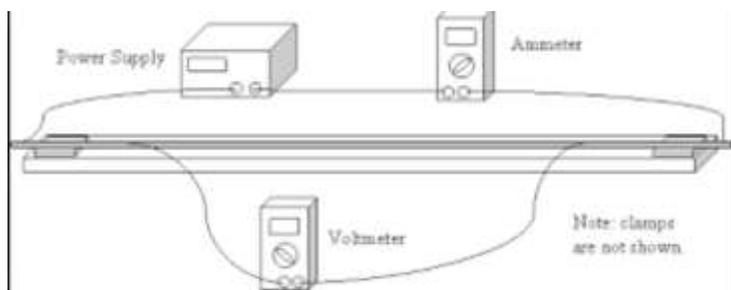
## Resistance and Ohm's Law

Give the equation for Ohm's law and show the rearrangements.


Use the diagram to explain how to investigate the factors affecting resistance:




# Revision Pack Topic P2- Electricity

Draw graphs showing voltage against current for each of the following components and explain what it shows.


Diode

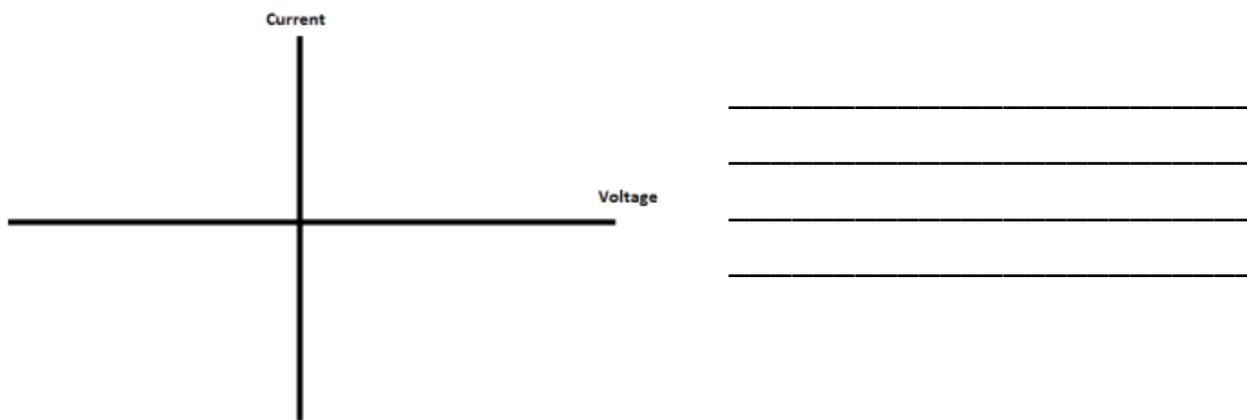

Filament Lamp

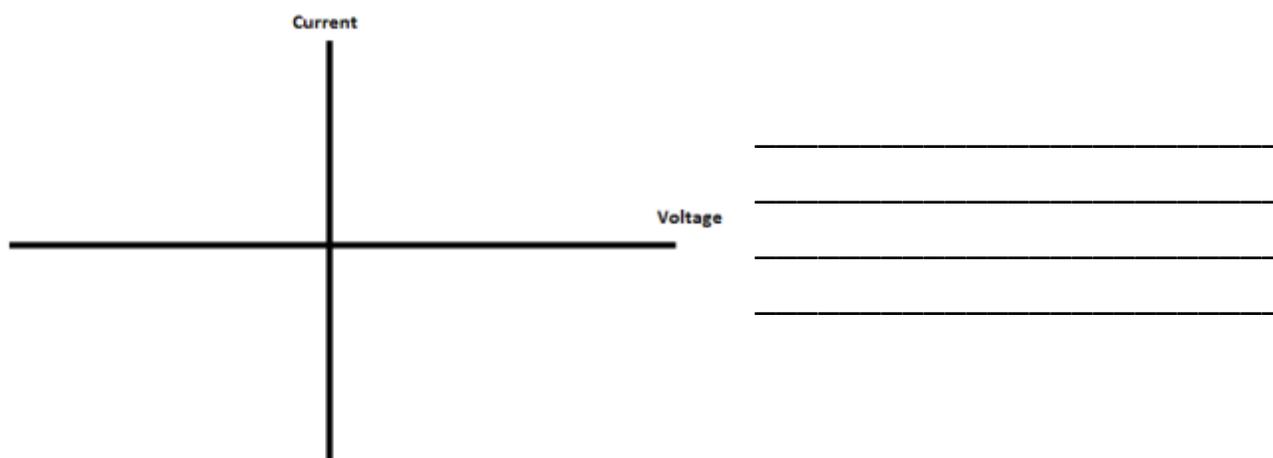

Fixed Resistor

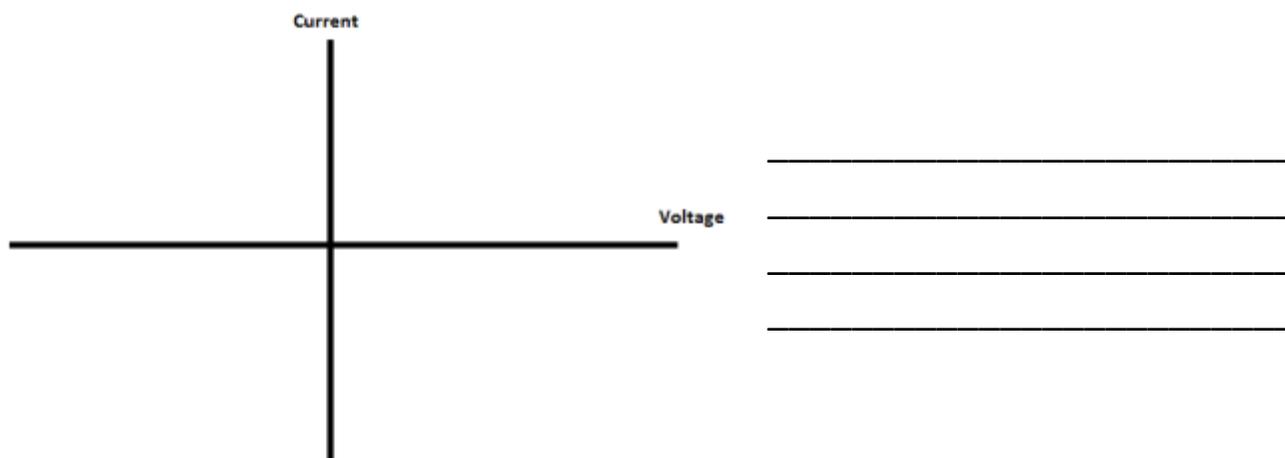

# Revision Pack Topic P2- Electricity

## Changing Resistance of LDRS and Thermistors

Thermistor

**Resistance**



**Temperature**

---

---

---

---

Light Dependent Resistor

**Resistance**



**Light Intensity**

---

---

---


---

# Revision Pack Topic P2- Electricity

## Series Circuits

Series – Means that all the components are connected in one loop.

## Current

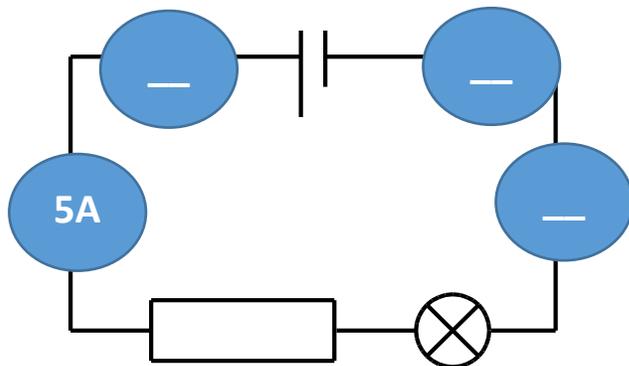

Label the diagram with the current at each point


## **Series Circuit Current Rule:**

Current is \_\_\_\_\_

Because \_\_\_\_\_

\_\_\_\_\_

## Voltage

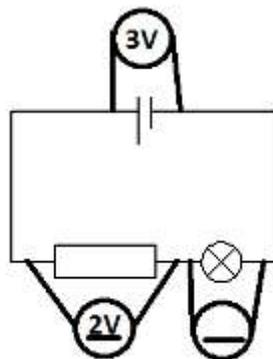

Label the diagram with the voltage at each point

## **Series Circuit Voltage Rule:**


Voltage is \_\_\_\_\_

Because \_\_\_\_\_

\_\_\_\_\_
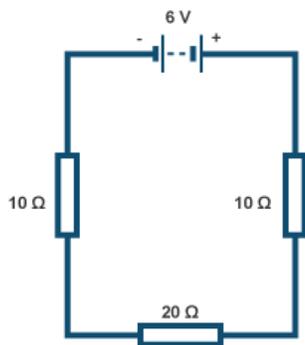
# Revision Pack Topic P2- Electricity


Calculating total resistance in a series circuit:



## Parallel Circuits

*Parallel – Means that the components are connected in multiple loops.*

## Current

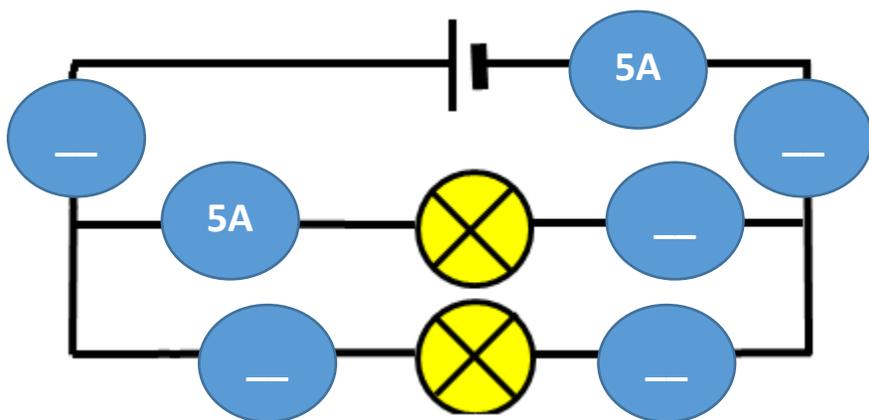

Label the diagram with the current at each point

**Parallel Circuit Current Rule:**


Current is \_\_\_\_\_

Because \_\_\_\_\_

\_\_\_\_\_.

# Revision Pack Topic P2- Electricity

## Voltage

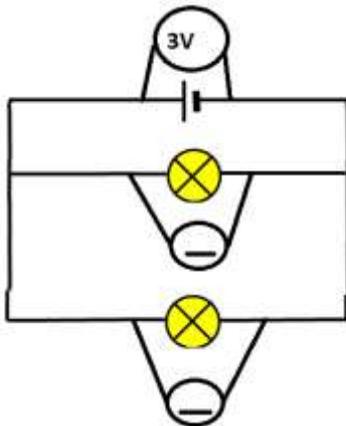

Label the diagram with the voltage at each point


### **Parallel Circuit Voltage Rule:**

Voltage is \_\_\_\_\_



Because \_\_\_\_\_

## Circuits in the home

Explain the features of a common plug:

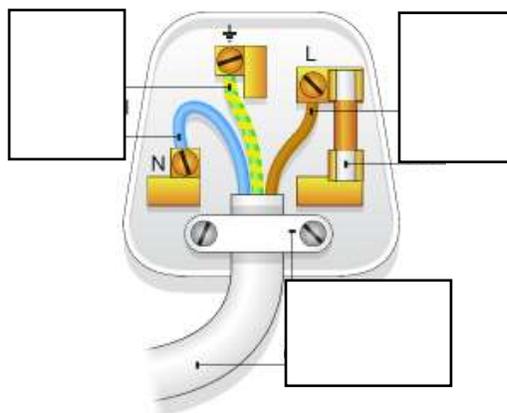

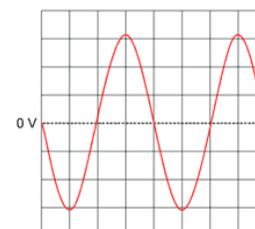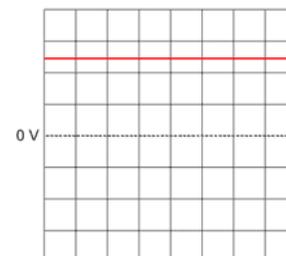Label the graphs to show the difference between A.C. and A.C.



# Revision Pack Topic P2- Electricity



Describe the energy transfers that take place when a kettle boils:



Describe the energy transfers that take place when a fan spins:

Give the two equations for calculating energy transferred:


Give the two equations for calculating power:

## The National Grid

What is the National Grid?

---

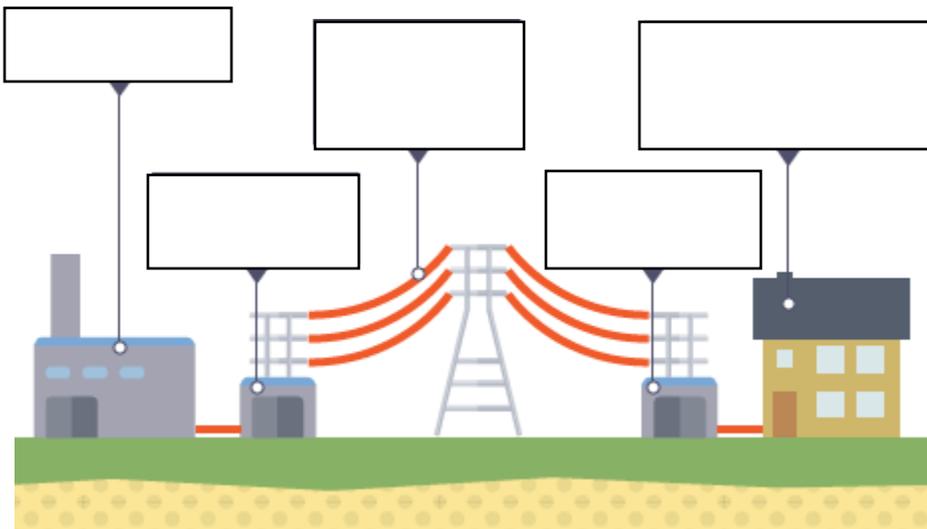
Use the diagram below to explain how the National Grid transports electricity to our homes. You should include information to explain the role of step up and step down transformers.



# Revision Pack Topic P2- Electricity

## Practice Exam Questions

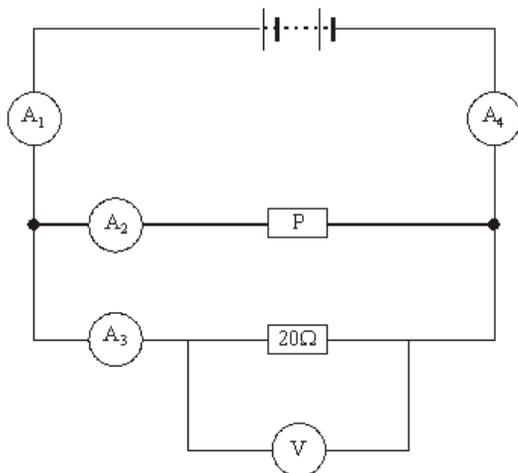**Q1.** The circuit shown has four identical ammeters.



(a) The table gives the current through two of the ammeters.

(i) Complete the table to show the current through the other two ammeters.

Ammeter	Reading on ammeter in amps
A <sub>1</sub>	
A <sub>2</sub>	0.2
A <sub>3</sub>	0.3
A <sub>4</sub>	

(2)

(ii) Which **one** of the following statements is correct. Tick (✓) the box next to your choice.

The resistance of **P** is more than 20 Ω.

The resistance of **P** is equal to 20 Ω.

The resistance of **P** is less than 20 Ω.

Give a reason for your choice.

.....

..... (2)

# Revision Pack Topic P2- Electricity

(b) (i) Write down the equation that links current, potential difference and resistance.

.....

(1)

(ii) Calculate the reading on the voltmeter. Show clearly how you work out your answer.

.....

.....

Voltmeter reading = ..... volts.


(2)

(iii) State the potential difference of the power supply.

.....

(1)

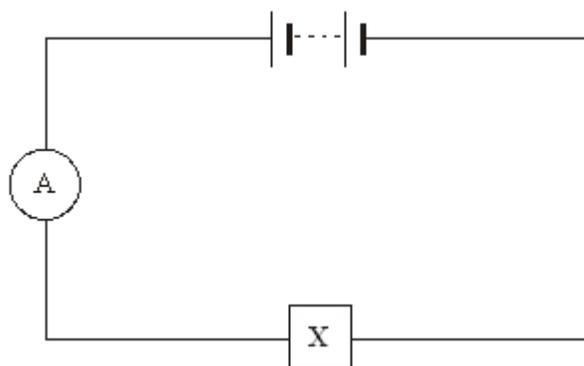(c) A second circuit contains an unknown component labelled **X**.



As component **X** is heated, the reading on the ammeter goes up.

What is component **X**?

.....

Give a reason for your answer.


.....

.....

(2)  
(Total 10 marks)

# Revision Pack Topic P2- Electricity

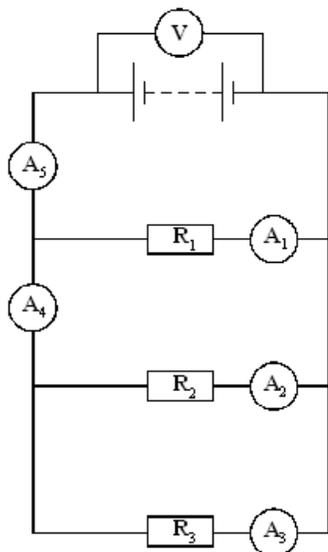Q2. A circuit was set up as shown in the diagram.



(a) The table gives the current through three of the ammeters. Complete the table to show the current through the other two ammeters.

Ammeter	Reading on ammeter in amps
$A_1$	0.2
$A_2$	0.6
$A_3$	0.3
$A_4$	
$A_5$	

(b) The reading on the voltmeter is 12 V.

What is the resistance of  $R_2$ ?

Show your working and include the correct unit.

.....

.....

.....

Resistance = .....

(2)

(3)

# Revision Pack Topic P2- Electricity

(c) In the circuit above, the resistor  $R_2$  burned out and current stopped flowing in it. There was no other change to the circuit. Complete the table below to show the readings on the ammeters after this took place.

Ammeter	Reading on ammeter in amps
$A_1$	0.2
$A_2$	0.0
$A_3$	
$A_4$	
$A_5$	

(3)

(Total 8 marks)

**Q3.** An electric current is a flow of electrical charge through a circuit.

(a) Complete the sentence. Use a word from the box.

atoms	electrons	ions	molecules
-------	-----------	------	-----------


Metals are good conductors of electricity because electrical charge is transferred by delocalised .....

(1)


(b) Draw **one** line from each symbol to the name of the component.

**Standard symbol**


**Name of component**

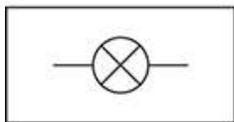

Battery

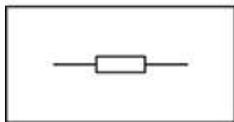

Lamp

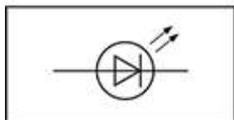

LED

Resistor

Switch

(3)

# Revision Pack Topic P2- Electricity

(c) The table below shows information about some electrical appliances.

Electrical appliance	Power in watts
 Hairdryer	1500
 Kettle	2500
 Electric hob	3000
 Television	360

A student plugs all four of the appliances into one multi-way socket.

The mains electricity is 230 V.

The highest safe current in the socket is 30 A.

Explain why it is not safe to use all four appliances at the same time.

In your answer you should:

- calculate the total power needed
- use the equation

$$\text{current} = \text{power} \div \text{potential difference}$$

to calculate the total current needed.


.....

.....

.....

# Revision Pack Topic P2- Electricity

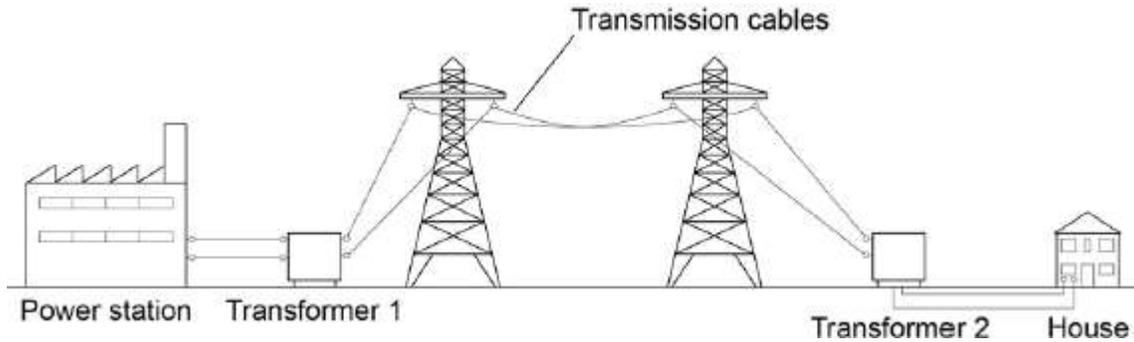- (d) The figure below shows how electrical power is transferred from power stations to consumers using the National Grid.



Transformer 1 is a step-up transformer.

Explain why step-up transformers are used in the National Grid.

.....

.....

.....

.....

(3)

- (e) What is the purpose of Transformer 2?

.....

.....

(1)

- (f) In a power station 900 MJ of thermal energy were released by burning natural gas.

Write down the equation that links efficiency, useful input energy transfer and useful output energy transfer.

.....

(1)

- (g) In a power station 900 MJ of thermal energy were released by burning natural gas.

Only 405 MJ was generated.

Calculate the efficiency of this energy transfer.

.....

.....

.....

Efficiency = .....(2)(Total 15 marks)

# Revision Pack Topic P2- Electricity

## Markscheme


M1. (a) (i)  $A_1 = 0.5$   
*ignore any units* 1

$A_2 = 0.5$   
*allow 1 mark for  $A_1 = A_2 \neq 0.5$*  1

(ii) the resistance of **P** is more than  $20 \Omega$  1

a smaller current goes through P /  $A_2$  (than  $20 \Omega$ )  
*dependent on getting 1<sup>st</sup> mark correct*  
*accept converse* 1

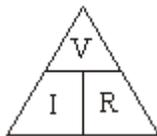(b) (i) potential difference = current  $\times$  resistance  
*accept pd / voltage for potential difference*  
*accept  $V = I \times R$ , correct symbols and correct case only*  
*accept volts = amps  $\times$  ohms*  
*accept*



*provided subsequent method is correct*  
*allow combination of*  
*physical quantities and named units*  
*allow voltage =  $I \times R$*  1

(ii) 6  
*allow 1 mark for correct substitution* 2

(iii) 6  
*accept their (b)(ii)* 1

(c) thermistor or



*accept correct circuit symbol*  
*allow phonetic spelling* 1

resistance goes down (as temperature of thermistor goes up)  
*do **not** accept changes for goes down*  
*do **not** accept an answer in terms of current only*  
 1

# Revision Pack Topic P2- Electricity

M2. (a) 0.9

1

1.1

*accept the value of  $A_4 + 0.2$*

1

(b)  $V = I R$  or  $12 = 0.6 R$  or  $\frac{12}{0.6} = ?$

*accept  $V = A R$   
 $V = I \times \text{ohm's sign}$   
do not credit Ohm's law triangle*

2

$R = 20$

*correct numerical answer earns both marks*

ohms

1

(c)  $A_3 = 0.3$

$A_4 = 0.3$

*accept the same numeric value as  $A_3$*

$A_5 = 0.5$

*accept the value of  $A_4 + 0.2$*


3

[8]

M3.(a) electrons

1

(b)

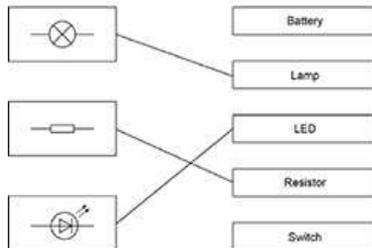

*extra lines from a symbol negate the mark*

3

(c) the total power = 7360 watts

1

current =  $7360 \div 230$

1

= 32 A

# Revision Pack Topic P2- Electricity

*allow 32 with no working shown for 3 marks*

- so the current is greater than 30 A 1
- (d) to increase the voltage (across the cables) or to decrease the current (through the cables) 1
- reducing energy losses (in the cables) 1  
*do not allow electricity for energy*  
*do not allow no energy loss*
- increasing the efficiency of transmission 1
- (e) to decrease the potential difference for domestic use 1
- (f)  $efficiency = \frac{useful\ output\ energy\ transfer}{total\ input\ energy\ transfer}$  1
- (g) 405 / 900 1
- =0.45 1  
*accept 45%*  
*allow 0.45 or 45% with no working shown for 2 marks*

[15]